

PMT, Base and Receiver Interface

Xiaoshan, Zhimin, Grewing, Robens

27th September 2016, Beijing


Protection

- There are three kind of large signals:
- Spark:
 - One of the high-voltage elements could have a discharge, worst case the signal point could drop by 2kV.
 - The signal-voltage would follow
 - With a good base design, spark should be very seldom, less than 1/Year?
 - High Bandwidth?
 - More resistors in serial to reduce the voltage across one element, that is the current design.
- Large signals from the PMT
 - The linearity of the Receiver is up to 1000 pe, setting the maximum input current at ca. 150mA
 - Measurements show currents up to 600mA. This can happen frequently (muons) with MCP-PMT. It must be simulated or measured if the signal bandwidth is lower (Time of flight variation)
- Ramp up of the HV
 - How fast will the HV ramp up?


Discussion on PMT base \leftrightarrow ADU interface

- Signal definition:
 - How much charge can the PMT give?
 - Capacitance of the PMT structure
 - Voltage over the capacitance?
 - PMT output measured:
 - Hamamatsu: 0~-8V with 1% overshoot on 50ohm
 - MCP PMT: 0~-32V with 1% overshoot on 50ohm
- What determines the bandwidth of large signals?
 - Variation of time of flight in the PMT
- What is the Bandwidth of the small signals
 - Measurements show 1.2ns,
 - Hamamatsu should be 2ns, which is the goal in order to get 2 samples on a rising edge


System Overview Discussion

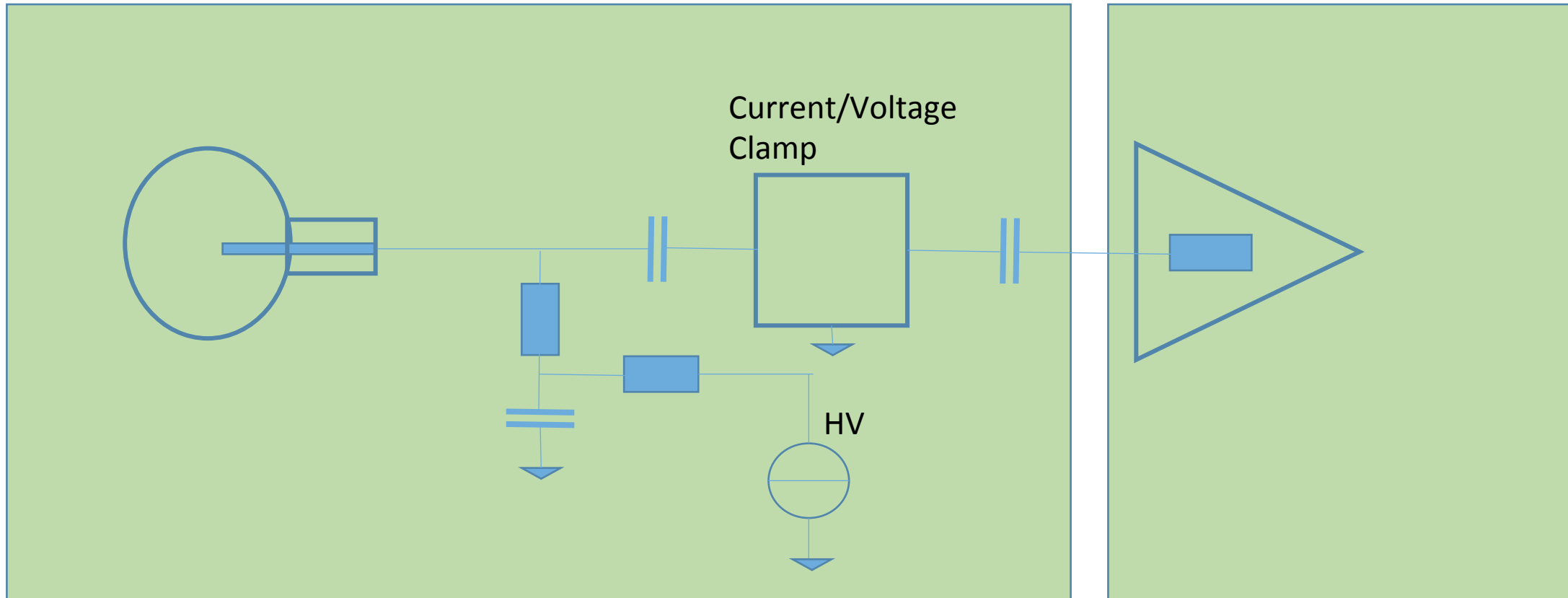


System Overview Discussion

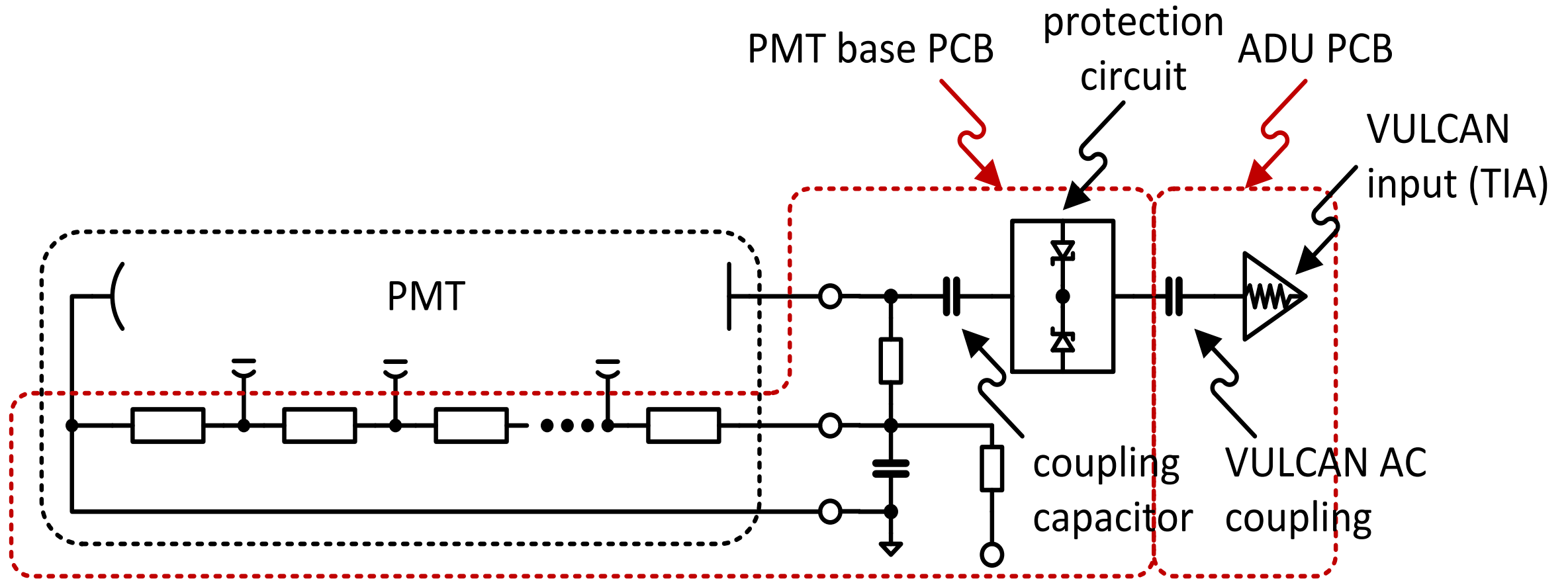


System Overview Discussion

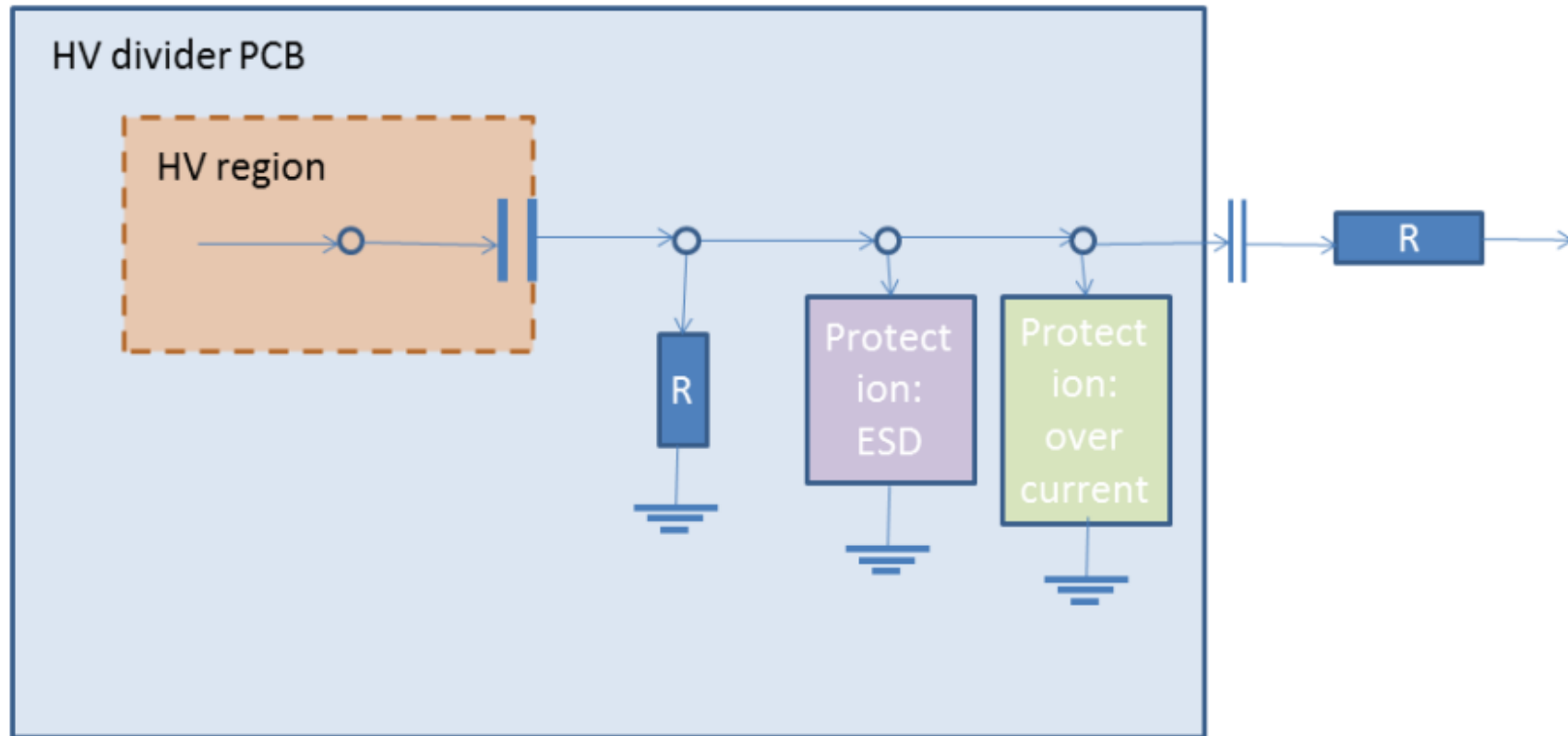

How does the clamp look like?

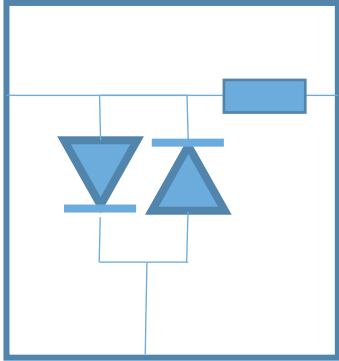

TVS with shunt resistor

 

TVS with shunt resistor
and highpass

- Approaches for protection
 - PSR: Pressure sensitive resistance
 - ESD: Electrostatic discharge
 - TVS: Transient voltage suppression
 - Arrester: <https://de.tdk.eu/inf/100/ds/S30-A75X-X1023T203.pdf>
- Questions:
 - Reliability?
 - What is the behavior if broken? (open/close)
 - Highvoltage behavior?
 - Resistorvalue?
 - Influence on Noise and OSC?
 - Signalshaping needs testing!
 - Capacitance should be $< 5\text{pF}$
 - Response time?
 - Variation of clamp voltages?

Open tasks

- Characterize the MCP-PMT in more detail. Probably it is a good idea to create a model of the MCP-PMT.
- Calculate total charge, a PMT may deliver.
- Do we need negative supply?
- Protection range will vary, which is the minimum range in relation to the needed linearity? (0-7.5 V at 50 Ohm to be discussed.)
- How much variation does each protection has?
- What is the time behaviour of the clamp and ESD? What pulses can the chip survive?
- Diodes would show better reliability, but will fail as a short.
- The value of the resistor is depending on the knee-voltage of the clamp (now the voltage is 7.5 – 8V)
- What is the parameter of the already designed protection of the chip (ESD)?
- Reliability of the Protection itself? (0.25% in 6 Years? Since the PMT is 0.5% in 6Years, does it has to be better? tbd)

Ideas for PMT signal limitation and protection

- Bird view of current protection ideas
 - ESD: HDM, MM to +/-4000V?
 - Limitation of output up limit to -160mA? And maximum current <-640mA?
 - How about overshoot?
- Protection design of current electronics
 - Valid range: 0~-160mA?
 - TIA: 0~-19.2mA. How about overshoot? Overshoot input is highohmic (0-3.3 V)
 - If the input current exceeds 20mA, the ESD protection will take the current, but not above 160mA.
 - What kind of protection already realized on electronics input? And parameters?
- Requirements to DC power from protection
 - If diode option: need ~7.3 V stable DC power and up to 640mA current pulse maximum? Must be buffered by capacitances.
 - Any voltage between 1.79- 20V is possible, what are the ripple requirements?
 - How about the reliability of the regulator, is it part of the base?
- Requirements to grounding
 - Need the grounding can handle 640mA current for over current and several 10s A for ESD?
- Possible options for ESD and over current, and how to avoid short if broken.


2016-09-27 Zhimin Wang

And comments from Robens and Steinmann

Summary of Action items:

- Reliability of arresters and TVA
- Simulation of the OSC with a train of pulses
- Design of OSC input
- Build a model of the PMT
- Size of the resistor in the clamp, in serial to the TIA input
- Calculate the resistance in the clamp and check noise behavior
- Check the ADC ranges: can the middle ADC range be changed to have a lower ADC range reference to catch the overshoot signal?

Discussion of the Design of OSC input

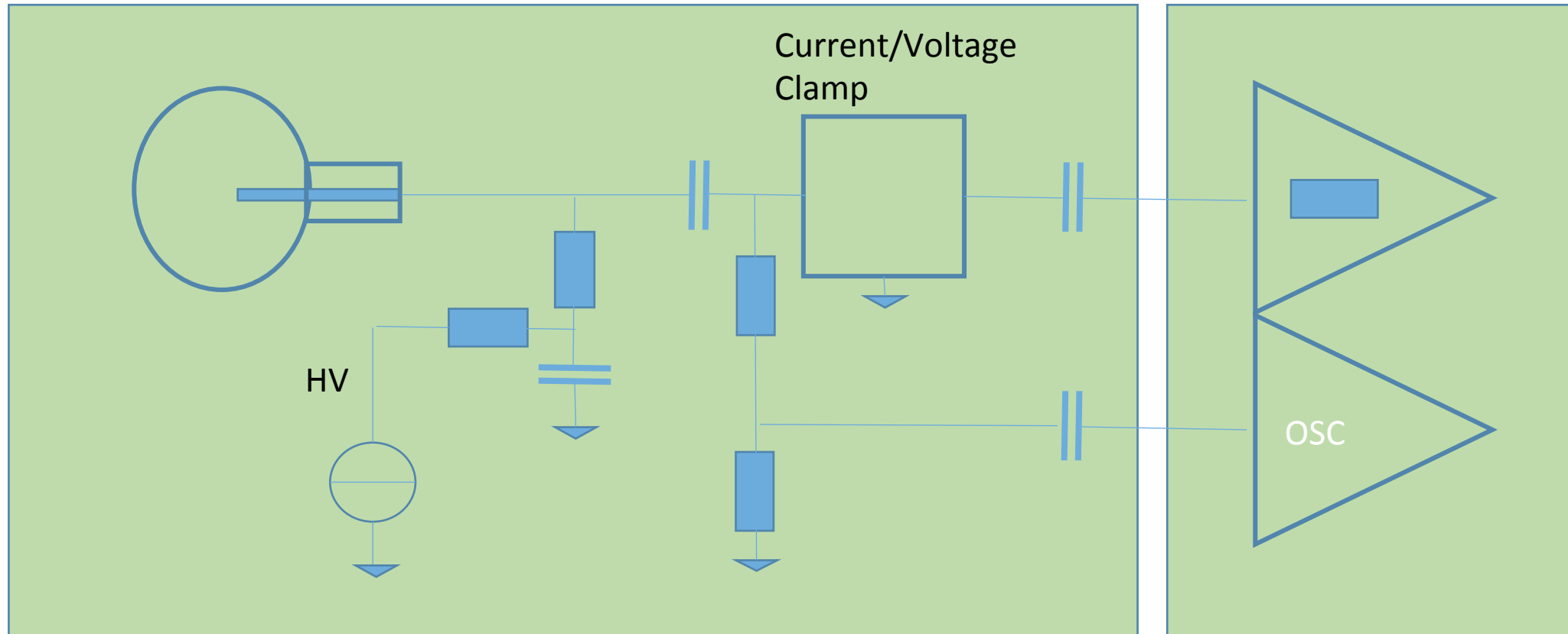

Build in selftest electronics

Vulcan can be programmed to send a test signal into the inputnode of the signal:

The DAC specification is:

$F_{clock} = 250\text{MHz}$

$V_{signal} = 0,1\text{V} - 0,9\text{V}$

The signal can be programmed with $256 * 8$ bit words

